

# Electronics World

www.electronicsworld.co.uk

July/August 2022

Volume 127

Issue 2019

£5.90

## Best applications for IoT in the world of IC power management



### SPECIAL REPORTS

- Medical electronics
- Power
- Processors
- Sensors
- Software

 **ANALOG  
DEVICES**

AHEAD OF WHAT'S POSSIBLE™

# Contents

## Regulars

### 04 Trend

### 05 Technology

### 10 Circuit Drill

By Sulaiman Algharbi Alsayed,  
Managing Director, Smart PCB Solutions

### 13 Optical Isolation

By Professor Murat Uzam, Department of  
Electrical and Electronics Engineering,  
Yozgat Bozok University, Turkey

### 41 Event

The Electronics Industry Awards 2022

### 48 Buyers' Guide

### 49 Products

### 50 Contact directory

### 51 Web locators

Cover supplied by Analog devices. More on pages 6-7

## Features

### 18 Advances in parallel processing with neuromorphic analogue chip implementations

By Alexander Timofeev, CEO and Founder,  
Polyn Technology

### 22 Latest technology and design trends shaping the power electronics industry

By Patrick Le Fèvre, Chief Marketing Officer, PRBX

### 26 IoT devices must rely on security-first approach

By Dennis Mattoon, Co-Chair, Trusted Computing  
Marketing Work Group, and Principal Software  
Engineer, Microsoft Research

### 28 The final frontier for global IoT

By Eric Hewitson, Business Development &  
Strategy Manager, Wyld Networks

### 32 Picking the right sensor for your industrial application

By Mathew Thorpe, Regional Sales Director for UK,  
Ireland and Benelux, Farnell

### 34 Electronic setups in the film and theatre industry

By Tony Ingham, Sales and Marketing,  
Sensor Technology

### 36 The right soldering atmosphere can mitigate soldering defects

By Rehm Thermal Systems's technical team

### 38 Drying: An essential step to cleaner PCBs for medical electronics

By Elizabeth Norwood, Senior Chemist,  
MicroCare



**ADVANCED INTERCONNECTIONS**  
THE POWER OF CUSTOM

Prototype to Production Volumes  
IC Sockets • Adapters • Board to Board Connectors

WWW.ADVANCED.COM • 800.424.9850

EDITOR: Svetlana Josifovska  
Tel: +44 (0)1732 883392  
Email: svetlanaj@electronicsworld.co.uk

SALES: Jack Wells  
Tel: +44 (0) 1622 699 171  
Email: jwells@datateam.co.uk

PRODUCTION/DESIGN: Tania King  
Email: tking@datateam.co.uk

MEDIA DIRECTOR: Louise Tiller  
Tel: +44 (0)1622 699104  
Email: ltiller@datateam.co.uk

ISSN: 1365-4675  
PRINTER: Buxton Press Ltd

SUBSCRIPTIONS:  
Subscription rates:  
1 year digital only - £40  
1 year print & digital (UK only) - £75  
1 year print & digital (Overseas) - £180  
Email: membership@electronicsworld.co.uk  
www.electronicworld.co.uk/subscribe

**datateam** Business Media 15A London Rd, Maidstone  
ME16 8LY, United Kingdom

Follow us on  
Twitter  
@electrow



Join us on  
LinkedIn



**EUROQUARTZ**  
ACCURATE  
SECURE  
TRACEABLE

See us at Engineering Design Show, Coventry Building Society Arena, October 12 & 13. Stand H4.

INDUSTRY SECTORS: DEFENCE | MEDICAL | AEROSPACE | COMMUNICATIONS | ELECTRONICS

IN-HOUSE PRODUCTION | UK-MADE SMD MILITARY AND INDUSTRIAL CLOCKS  
5G OSCILLATORS | MICRO-MINIATURE | OCXOs | TCXOs | VCXOs | ITAR-FREE OSCILLATORS

📞: +44(0)1460 230000 | 📧: sales@euroquartz.co.uk | 🌐: www.euroquartz.co.uk

# Optically-isolated input modules for a -10V to +10V to 0-5V signal converter

By Professor Murat Uzam, Department of Electrical and Electronics Engineering, Yozgat Bozok University, Turkey

In this month's column we will cover two optically-isolated analogue input modules for a -10V to +10V to 0-5V signal converter, with DC input voltages varying between -12V and +12V, powered by +5.00V, +6.26V, -12V, +12V, +12V (isolated) for module 1 and -12V, +12V and +12V (isolated) for module 2.

### Module 1

Figure 1 shows the -10V - +10V to 0-5V signal converter for use with the ADC input of a 5V microcontroller; its connections are shown in Figure 2. The circuit is based on the Positive Unipolar Photovoltaic Isolation Amplifier 1 (PUPIA1 – explained in a previous month), with an HCNR201 high-linearity analogue optocoupler for photovoltaic isolation. The circuit's output is isolated from  $V_{IN}$ .

This design is used to level-shift the bipolar -10V - +10V analogue input signals to provide a unipolar 0-5V signal. The

transfer function is obtained from:

$$V_{OUT} = \left( \frac{R1 \cdot R3}{R2 + R1 \cdot R3} \right) V_{IN} + \left( \frac{R2 \cdot R3}{R1 + R2 \cdot R3} \right) 5$$

Since  $R2 = R3$ ,  $R1 = \frac{1}{2} R2$ ,

$$V_{OUT} = \left( \frac{1}{4} \right) V_{IN} + \left( \frac{1}{2} \right) 5 = \frac{V_{IN} + 10}{4}$$

$V_{IN}$  can be subjected to electric surge or electrostatic discharge on the external terminal connections, but adding a transient voltage suppressor (TVS) gives it good protection. A ferrite bead is connected in series with the input path to add isolation and decoupling from high-frequency transient noises. External Schottky diodes protect the operational amplifier. Even when internal ESD protection diodes are present, using external diodes lowers noise and offsets errors. Dual series Schottky barrier diodes D1 and D2 divert any overcurrent to the positive or negative power supply. External Schottky diodes D3 and D4 protect the operational amplifier. Even when internal ESD protection diodes are present, using external diodes lowers noise and offsets errors. Dual series Schottky barrier diodes D1 and D2 divert any overcurrent to the positive or negative power supply.

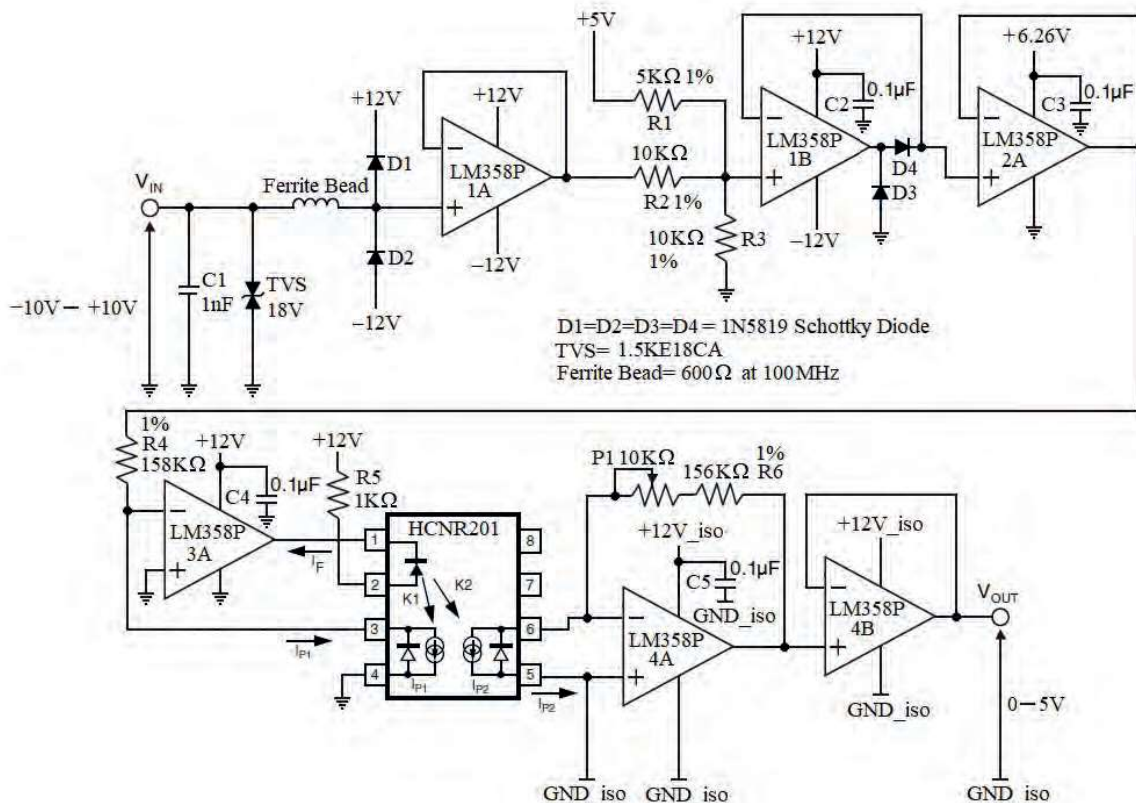


Figure 1: -10V - +10V to 0-5V signal converter – module 1

The operational amplifier LM358P-1A, with bipolar supply voltages, provides a high input impedance and is connected as a buffer amplifier (voltage follower).

Diodes D3 and D4 ensure that when  $-12.00V \leq V_{IN} < -10.00V$ ,  $V_{OUT} = 0.00V$ . The operational amplifier LM358P-2A, with a +6.26V supply voltage, acts as a voltage limiter and is connected as a buffer amplifier. Its output is connected to the input of PUIA1, limited by LM358P-1A.

Here, PUIA1 consists of:

1. Input section: R4, R5, C4, LM358P-3A;
2. HCNR201 high-linearity analogue optocoupler;
3. Output section: P1, R6, C5, LM358P-4A.

In this design, the circuit's input is powered by +5.00V, +6.26V, -12V and -12V. Likewise, the circuit's output is powered by +12V isolated from the input. The output of the PUIA1 is connected to the non-inverting input terminal of the buffer amplifier LM358P-4B, obtaining  $V_{OUT}$ .

We assume  $V_{IN}$  is  $-12V$  to  $+12V$ . When  $-12.00V \leq V_{IN} < -10.00V$ ,  $V_{OUT} = 0.00V$ . When  $-10.00V \leq V_{IN} \leq +10.00V$ ,  $V_{OUT} = (V_{IN} + 10V) / 4$ . When  $+10.01V \leq V_{IN} \leq +12V$ ,  $V_{OUT}$  will be a value from 5.01V to 5.07V, due to LM358P-2A. See  $V_{OUT}$  vs  $V_{IN}$  in Figure 3, with some examples in Table 1.

For proper operation make  $R2 = R3$ ,  $R1 = \frac{1}{2}R2$  and  $+5V = +5.00V$ .

To calibrate the setup, set  $V_{IN}$  to  $+10.00V$  and adjust P1 to bring  $V_{OUT}$  to  $+5.00V$ .

**Module 2**

Figures 5, 6 and 7 show the optically-isolated analogue input module 2 with its connections to the ADC port of a 5V microcontroller. As before, this circuit is also PUIA1-based, with a high-linearity analogue optocoupler (HCNR201) providing photovoltaic isolation.

This design is used to level-shift the bipolar  $-10V$  -  $+10V$  analogue voltage signal to provide a unipolar input of 0-5V.

The transfer function is obtained from the following:

$$V_{OUT} = \left( \frac{R1 \cdot R3}{R1 + R3} \right) V_{IN} + \left( \frac{R2 \cdot R3}{R1 + R2 + R3} \right) 5$$


Since  $R2 = R3$ ,  $R1 = \frac{1}{2}R2$ ,

$$V_{OUT} = \left( \frac{1}{4} \right) V_{IN} + \left( \frac{1}{2} \right) 5 = \frac{V_{IN} + 10}{4}$$

R7, D5 (10V zener diode) and C6 provide a 10.00V reference voltage from +12V. This 10.00V is divided with R8 and R9 to obtain +5.00V, which can source current to 20mA.

Likewise, the 10.00V reference voltage is also divided by using R10 and R11 to obtain a +6.26V reference voltage. Next, the 5V is connected to the non-inverting input of the buffer amplifier LM358P-3B, whose output is fixed at 5V, sourcing current to 20mA.

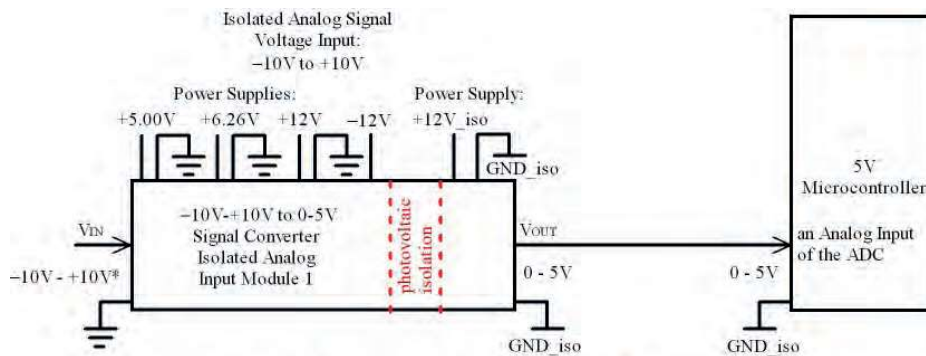$V_{IN}$  can be subjected to electric surge or electrostatic discharge on the external terminal connections; the TVS (transient voltage suppressor) protects it. Dual series



\*: Input voltage values from  $-12V$  to  $+12V$  are accepted without any damage.  
 When  $-12.00V \leq V_{IN} < -10.00V$ ,  $V_{OUT} = 0.00V$ .  
 When  $-10.00V \leq V_{IN} \leq +10.00V$ ,  $V_{OUT} = (V_{IN} + 10V) / 4$ .  
 When  $+10.01V \leq V_{IN} \leq +12V$ ,  $V_{OUT}$  will be equal to a value from 5.01V to 5.07V.

Figure 2: Function generator signals when none of the outputs are connected to a load

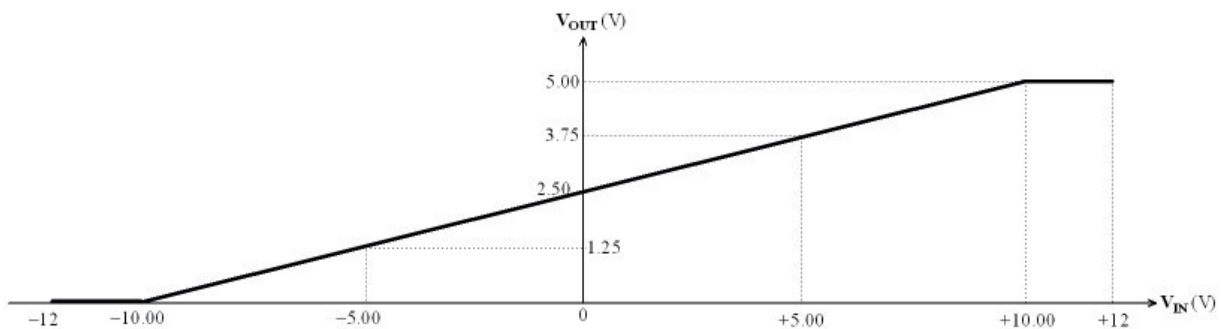


Figure 3:  $V_{OUT}$  vs.  $V_{IN}$  relationship for modules 1 and 2

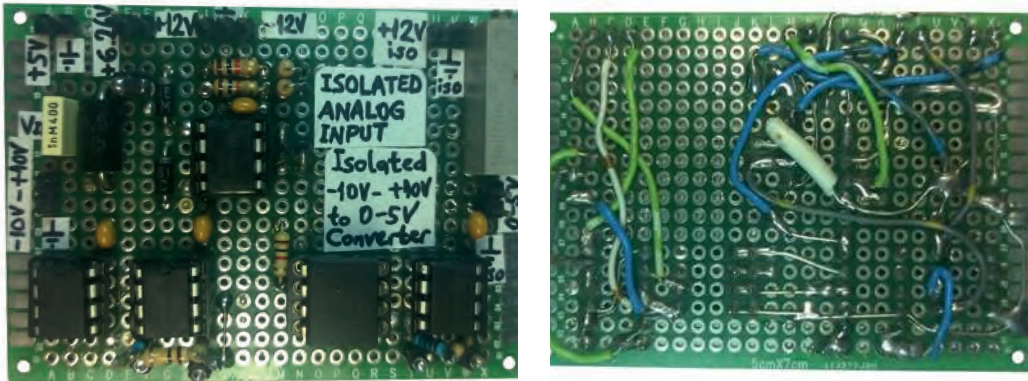


Figure 4: Module 1's prototype circuit board

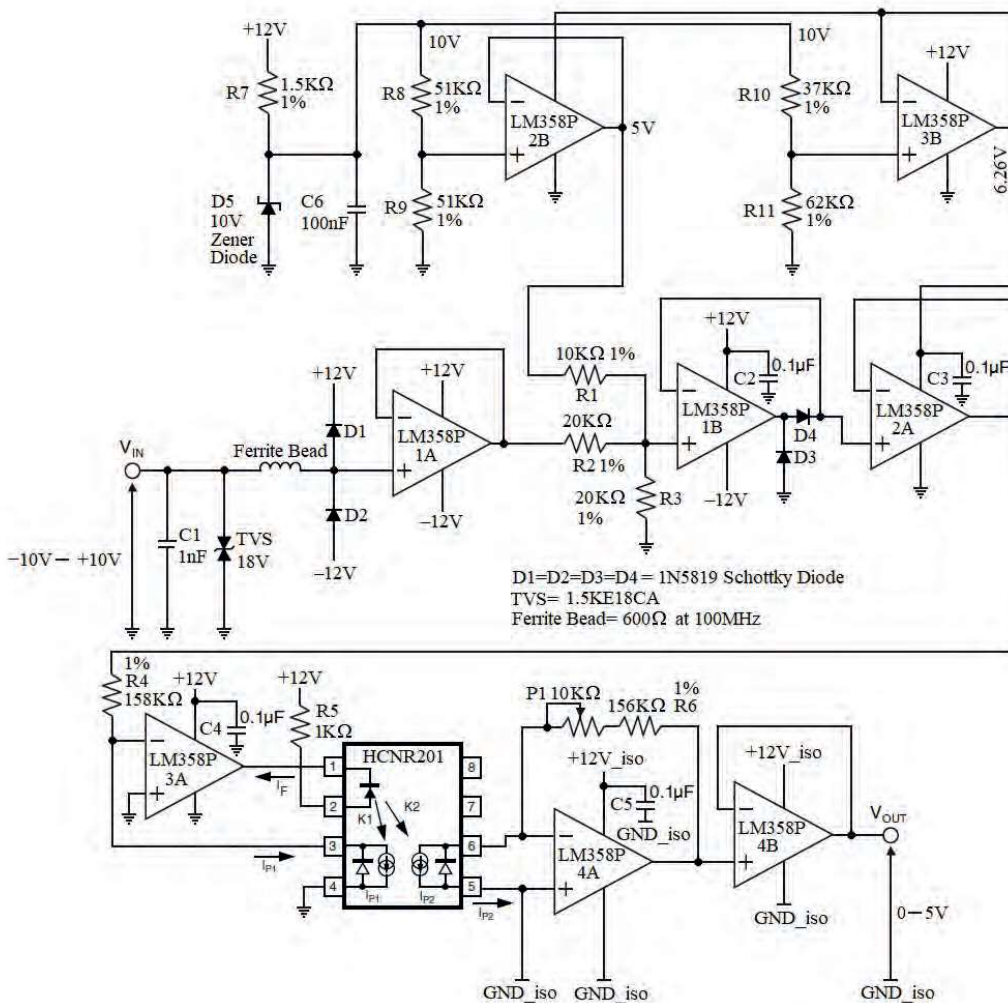


Figure 5: Module 2

V <sub>in</sub> (V)	V <sub>out</sub> (V)
+12.00	5.0X
..	5.0X
+11.00	5.0X
..	5.0X
+10.00	5.00
..	..
+9.00	4.75
..	..
+8.00	4.50
..	..
+7.00	4.25
..	..
+6.00	4.00
..	..
+5.00	3.75
..	..
+4.00	3.50
..	..
+2.00	3.00
..	..
0.00	2.50
..	..
-1.00	2.25
..	..
-3.00	1.75
..	..
-4.00	1.50
..	..
-5.00	1.25
..	..
-6.00	1.00
..	..
-7.00	0.75
..	..
-8.00	0.50
..	..
-9.00	0.25
..	..
-10.00	0.00
..	..
-11.00	0.00
..	..
-12.00	0.00

Table 1: Example input and output voltages for modules 1 and 2 (5.0X: a value from 5.01V to 5.07V)

Schottky barrier diodes D1 and D2 divert any overcurrent to the positive or negative power supply.

The operational amplifier LM358P-1A, with bipolar supply voltages, provides a high input impedance and is connected as a buffer amplifier (voltage follower). Diodes D3 and D4 ensure that when  $-12.00V \leq V_{IN} < -10.00V$ ,  $V_{OUT} = 0.00V$ . The operational amplifier LM358P-2A, with a +6.26V

supply voltage, acts as a voltage limiter and is connected as a buffer amplifier.

LM358P-2A's output is connected to PUIPIA1's input, which limits the input voltage. PUIPIA1 consists of:

1. Input section: R4, R5, C4, LM358P-3A;
2. HCNR201 high-linearity analogue optocoupler;
3. Output section: P1, R6, C5, LM358P-4A.

The input and output are powered by isolated +12V. It is assumed that  $V_{IN} = -12V$  to +12V. When  $-12.00V \leq V_{IN} < -10.00V$ ,  $V_{OUT} = 0.00V$ . When  $-10.00V \leq V_{IN} \leq +10.00V$ ,  $V_{OUT} = (V_{IN} + 10V) / 4$ . When  $+10.01V \leq V_{IN} \leq +12V$ ,  $V_{OUT}$  will be a value from 5.01V to 5.07V, because of LM358P-2A; see Figure 3 and Table 1.

For proper operation make  $R2 = R3$ ,  $R1 = \frac{1}{2} R2$ ,  $R8 = R9$ , and  $R11/(R10+R11) = 62.62\%$ . **EW**

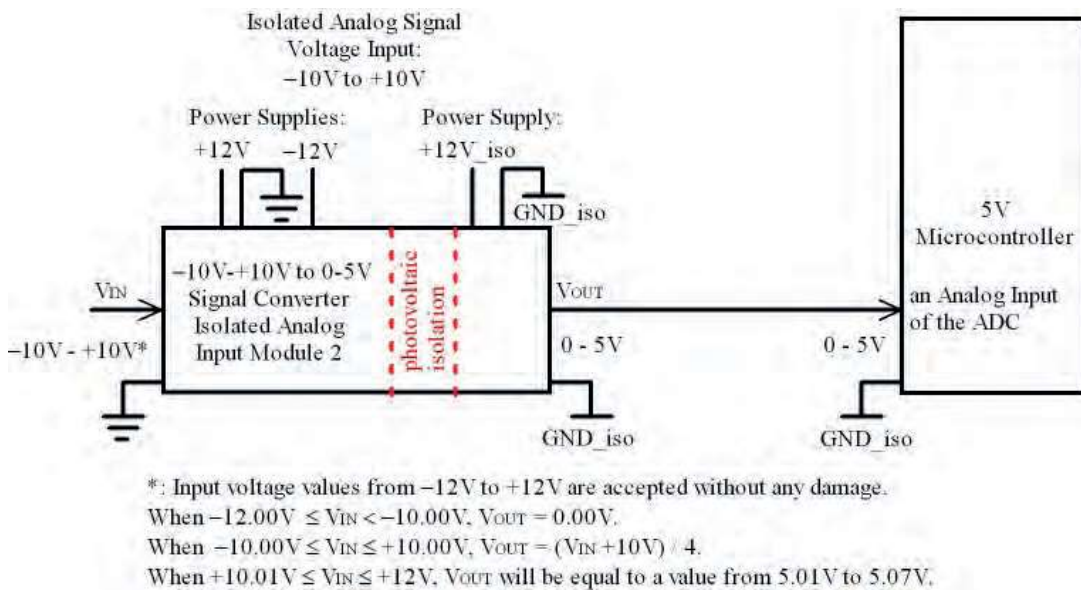


Figure 6: Module 2's connections

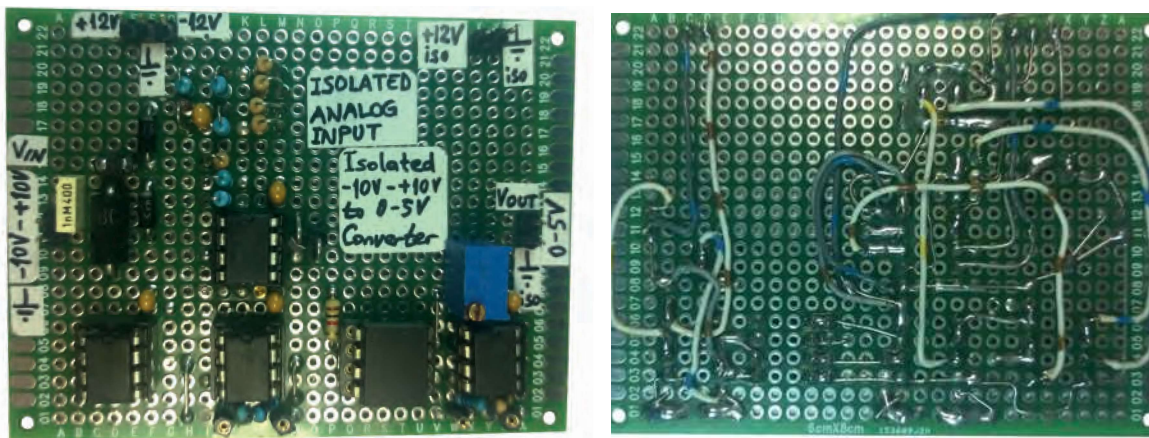


Figure 7: Module 2's prototype circuit board