

Electronics World

www.electronicworld.co.uk

September 2022

Volume 127

Issue 2020

£5.90



RIGOL

StationMax
Oscilloscope –
In a class of its own

SPECIAL REPORTS

- Communications design
- Industrial electronics
- System security
- Wearable devices design
- MOSFETs

Contents

Regulars

04 Trend

05 Technology

08 NEW REGULAR EMC

Considerations for EMI filter design

By REO UK design engineers and Dr Min Zhang, EMC consultant, Mach One Design

10 Circuit Drill

By Sulaiman Algharbi Alsayed, Managing Director, Smart PCB Solutions

12 NEW REGULAR Electric Vehicles

By Vicor design engineers

14 Optical isolation

By Professor Murat Uzam, Department of Electrical and Electronics Engineering, Yozgat Bozok University, Turkey

31 Event

The Electronics Industry Awards 2022

36 Products

38 Contact directory

39 Web locators

Cover supplied by Rochester Electronics. More on pages 6-7



Features

17 Highly-secure embedded CPUs for the needs of edge servers

By Electronics World editors

20 Building power supplies for battery-powered IIoT sensors

By Rolf Horn, Applications Engineer, Digi-Key Electronics

23 The time for Wi-Fi 6 is now!

By Dominikus Hierl, SVP of Sales for EMEA, Quectel

24 Combining the benefits of true time delays and phase shifters

By Bilgin Kiziltas, Field Applications Engineer, Analog Devices

28 Wearables – more than just fitness trackers

By Sara Urasini, Head of Wearables, Design Partners, part of PA Consulting

30 The end of the (production) line for the lateral MOSFET

By Profusion technical staff

ADVANCED INTERCONNECTIONS
THE POWER OF CUSTOM

Prototype to Production Volumes
IC Sockets • Adapters • Board to Board Connectors

WWW.ADVANCED.COM • 800.424.9850

EDITOR: Svetlana Josifovska
Tel: +44 (0)1732 883392
Email: svetlanaj@electronicsworld.co.uk

SALES: Kalil Kayani
Tel: +44 (0)1622 699129
Email: KKayani@datateam.co.uk

PRODUCTION/DESIGN: Tania King
Email: tking@datateam.co.uk

MEDIA DIRECTOR: Louise Tiller
Tel: +44 (0)1622 699104
Email: ltiller@datateam.co.uk

ISSN: 1365-4675
PRINTER: Buxton Press Ltd

SUBSCRIPTIONS:
Subscription rates:
1 year digital only - £40
1 year print & digital (UK only) - £75
1 year print & digital (Overseas) - £180
Email: membership@electronicsworld.co.uk
www.electronicworld.co.uk/subscribe

datateam Business Media
15A London Rd, Maidstone
ME16 8LY, United Kingdom

Follow us on
Twitter
@electrowo



Join us on
LinkedIn




EUROQUARTZ
ACCURATE
SECURE
TRACEABLE

See us at Engineering Design Show, Coventry Building Society Arena, October 12 & 13. Stand H4.

ENGINEERING DESIGN SHOW

ISO 9001 REGISTERED
UKAS MANAGEMENT SYSTEMS

INDUSTRY SECTORS: DEFENCE | MEDICAL | AEROSPACE | COMMUNICATIONS | ELECTRONICS

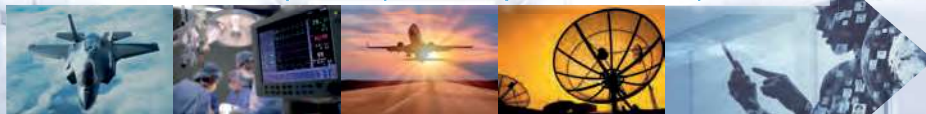

IN-HOUSE PRODUCTION | UK-MADE SMD MILITARY AND INDUSTRIAL CLOCKS
5G OSCILLATORS | MICRO-MINIATURE | OCXOs | TCXOs | VCXOs | ITAR-FREE OSCILLATORS

t: +44(0)1460 230000 | e: sales@euroquartz.co.uk | w: www.euroquartz.co.uk

Optically-isolated input modules for a 0-5V or 4-20mA to 0-5V signal converter

By Professor Murat Uzam, Department of Electrical and Electronics Engineering, Yozgat Bozok University, Turkey

In this month's column we will cover two optically-isolated analogue input modules for a 0-5V or 4-20mA to 0-5V signal converter. Module 1 (Figure 1) handles DC input voltages from 0V to +12V, or DC input currents from 0mA to 48mA, and requires DC power supplies of +6.26V, +12V and isolated +12V. Module 2 handles the same input voltages and currents but requires DC power supplies of +12V and isolated +12V.

Figure 2 shows Module 1's connections to an analogue input of a 5V microcontroller. This circuit contains the Positive Unipolar Photovoltaic Isolation Amplifier 1 (PUPIA1 – explained previously), with HCNR201 high-linearity analogue optocoupler for photovoltaic isolation.

The circuit's output, to the right of the HCNR201, is isolated from V_{IN} , to the left. Here we assume that when the voltage mode is selected, V_{IN} is between 0 and 12V, and when the current mode is selected, I_{IN} is between 0 and 48mA.

In voltage mode (S1 open), when $0.00V \leq V_{IN} \leq 5.00V$, $V_{OUT} = V_{IN}$. When $5.01V \leq V_{IN} \leq 12V$, V_{OUT} will be a value

from 5.01V to 5.07V, due to the electrical characteristics of the LM358P-1A.

In current mode (S1 closed), when $0mA \leq I_{IN} \leq 20mA$, $V_{OUT} = (I_{IN} \cdot 250)V$. When $20mA < I_{IN} \leq 48mA$, V_{OUT} will be a value from 5.01V to 5.07V, again because of the LM358P-1A.

The curves V_{OUT} vs V_{IN} and I_{IN} are shown in Figure 3; it can be seen that for input voltages to 12V and input currents to 48mA the circuit suffers no damage.

V_{IN} and I_{IN} can be subjected to electric surge or electrostatic discharge on the circuit's external terminal connections, but the TVS (transient voltage suppressor) provides highly-effective protection. D1 protects the circuit from accidental reverse polarity of V_{IN} or I_{IN} .

Jumper S1 (shown here as a switch) switches between current and voltage, with $R1 = 250\Omega$ used to adjust the levels. When S1 is open, the input can be 0-5V; when closed, the input can be 0-20mA.

A ferrite bead in series with the input path adds isolation and decoupling from high-frequency transient noises, whereas external Schottky diodes protect the op-amp. Even with internal ESD protection diodes, it's recommended to use external diodes since they lower noise and offset errors in the circuit.

Dual series Schottky barrier diodes D2 and D3 divert overcurrents to ground or the power supply. With its +6.26V power, the LM358P-1A op-amp acts as a voltage limiter, provides a high input impedance and is connected as a buffer amplifier (voltage follower). Its output is connected to the PUPIA1's input, limiting the input voltage.

Here, PUPIA1 consists of:

1. Input section: R2, R3, C3, LM358P-2A.
2. HCNR201 high-linearity analogue optocoupler.

3. Output section: P1, R4, C4, LM358P-3A. In this design, the circuit's input section is powered by +6.26V and +12V; likewise, the output part is powered by another +12V power supply, isolated from the input. PUPIA1's output is connected to the non-inverting input of the buffer amplifier LM358P-3B. Output voltage V_{OUT} is thus obtained from the output of LM358P-3B.

Table 1 shows some example input and output voltages and currents for Modules 1

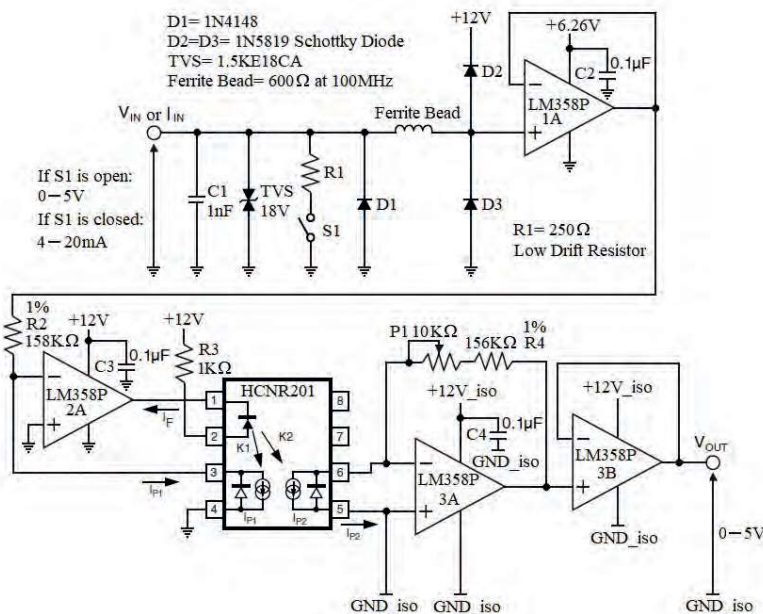


Figure 1: Module 1


and 2, with Figure 4 showing the PCB.

Circuit calibration is carried out with S1 open: set V_{IN} to +5.00V and V_{OUT} to +5.00V by adjusting P1.

Module 2

Figures 5, 6 and 7 show the optically-isolated analogue input module 2, with its connections to the ADC port of a 5V microcontroller. The circuit is also PUIIA1-based, with a high-linearity analogue optocoupler (HCNR201) providing photovoltaic isolation.

Module 2 operates exactly the same way as module 1, using the same components, but with R5, D4 (10V zener diode) and C5 added, which provide 10.00V reference voltage from a +12V power supply. The 10.00V reference is then divided with R6 and R7 to obtain +6.26V. This reference voltage is then connected to the non-inverting input of buffer amplifier LM358P-2B, with output fixed at +6.26V and sourcing to 20mA. For proper operation ensure that $R7/(R6+R7) = 62.62\%$. [EW](#)

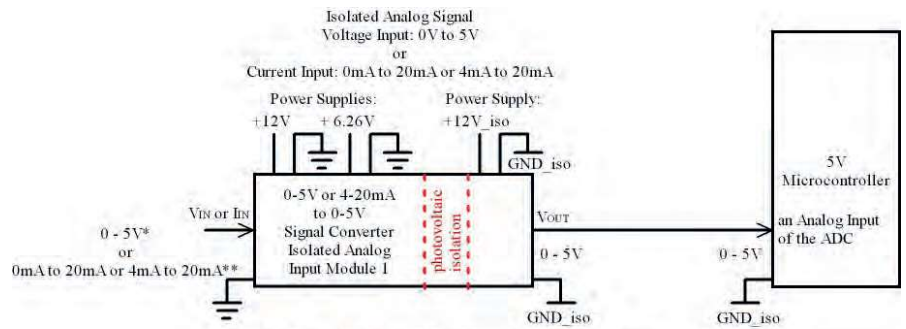

*: Input voltage values up to 12V are accepted without any damage.
 When $0.00V \leq V_{IN} \leq 5.00V$, $V_{OUT} = V_{IN}$.
 When $5.01V \leq V_{IN} \leq 12V$, V_{OUT} will be equal to a value from 5.01V to 5.07V.
 **: Input current values up to 48mA are accepted without any damage.
 When $0mA \leq I_{IN} \leq 20mA$, $V_{OUT} = (I_{IN} \cdot 250)V$.
 When $20mA < I_{IN} \leq 48mA$, V_{OUT} will be equal to a value from 5.01V to 5.07V.

Figure 2: Module 1's connections to an MCU

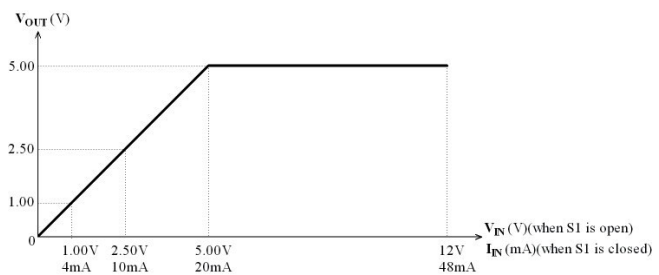


Figure 3: V_{OUT} vs. V_{IN} for modules 1 and 2

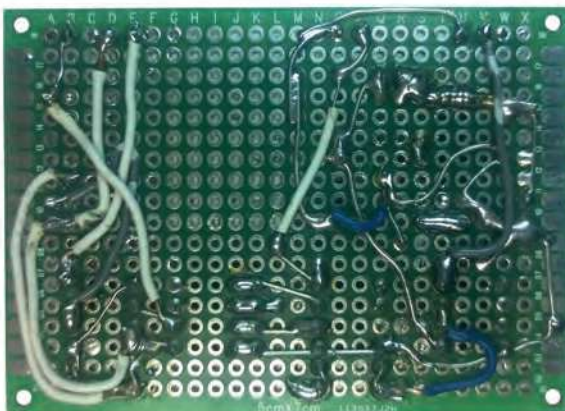
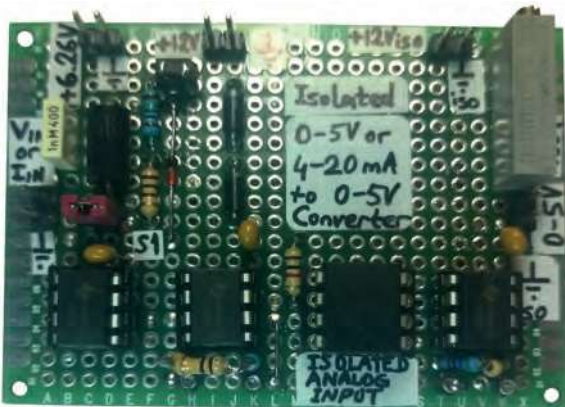


Figure 4: Module 1's PCB


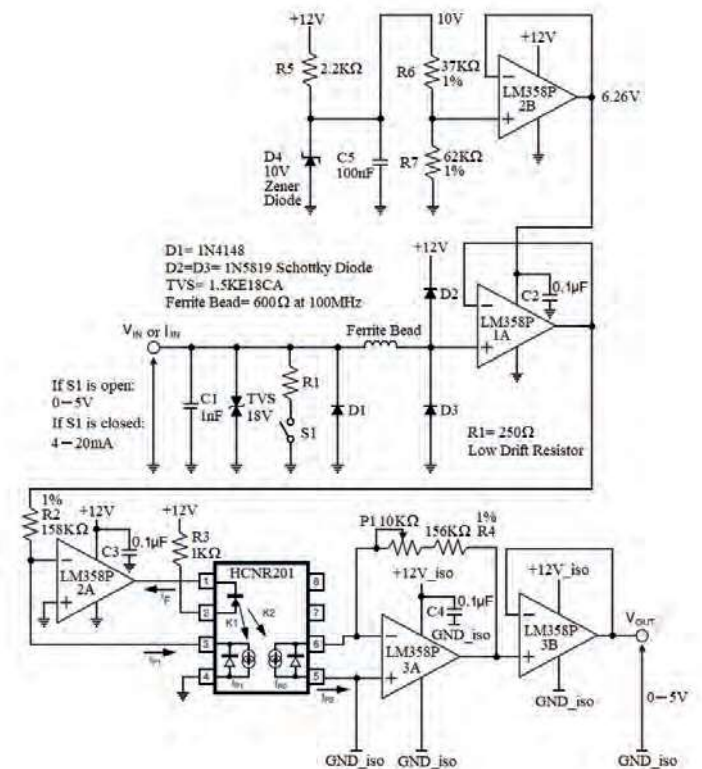


Figure 5: Module 2

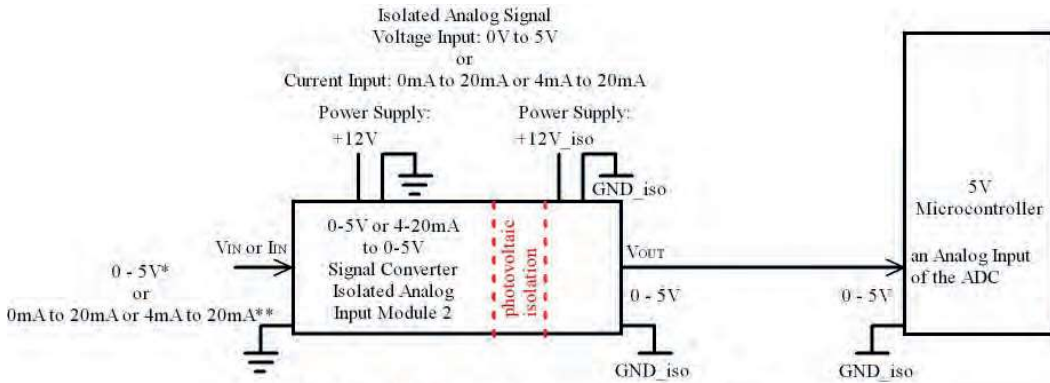

*: Input voltage values up to 12V are accepted without any damage.
 When $0.00V \leq V_{IN} \leq 5.00V$, $V_{OUT} = V_{IN}$.
 When $5.01V \leq V_{IN} \leq 12V$, V_{OUT} will be equal to a value from 5.01V to 5.07V.
 **: Input current values up to 48mA are accepted without any damage.
 When $0mA \leq I_{IN} \leq 20mA$, $V_{OUT} = (I_{IN} \cdot 250)V$.
 When $20mA < I_{IN} \leq 48mA$, V_{OUT} will be equal to a value from 5.01V to 5.07V.

$V_{IN}(V)$	$I_{IN}(mA)$	$V_{OUT}(V)$
12.00	48	5.0X
..	..	5.0X
10.00	40	5.0X
..	..	5.0X
5.00	20	5.00
..
4.75	19	4.75
..
4.50	18	4.50
..
4.25	17	4.25
..
4.00	16	4.00
..
3.75	15	3.75
..
3.50	14	3.50
..
3.25	13	3.25
..
3.00	12	3.00
..
2.75	11	2.75
..
2.50	10	2.50
..
2.25	9	2.25
..
2.00	8	2.00
..
1.50	6	1.50
..
1.25	5	1.25
..
1.00	4	1.00
..
0.75	3	0.75
..
0.50	2	0.50
..
0.25	1	0.25
..
0.00	0.00	0.00

Table 1: Example input and output voltages for Modules 1 and 2 (5.0X: a value from 5.01V to 5.07V)

Figure 6: Module 2's connections

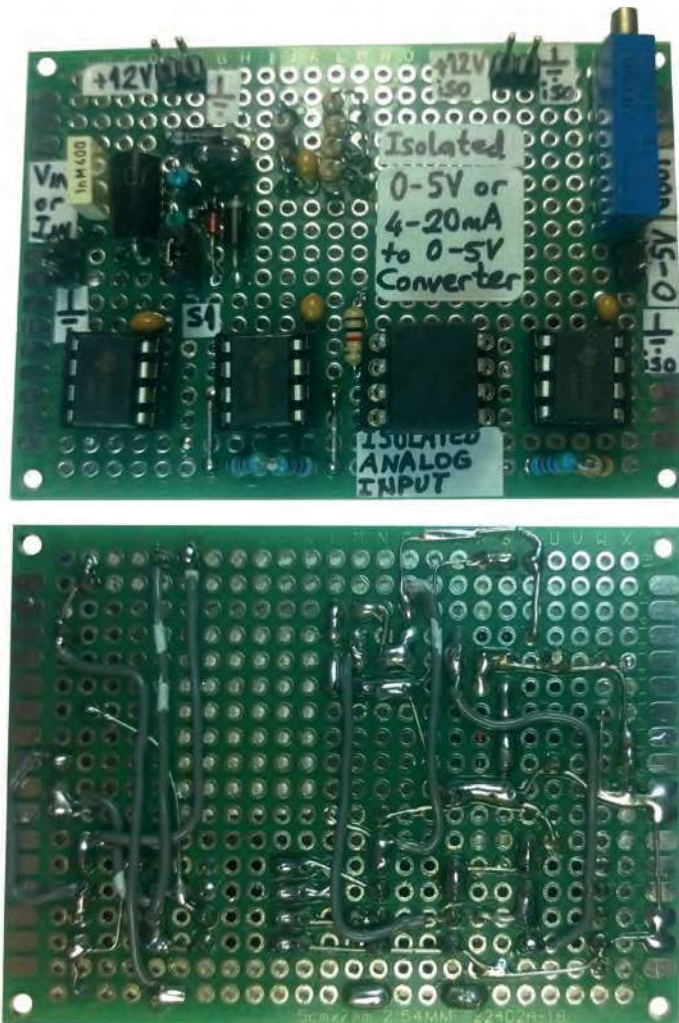


Figure 7: Module 2's PCB